



GFM Inverter Interoperability Through Hardware Testing

Jing Wang, Subhankar Ganguly, and Soham Chakraborty
National Renewable Energy Laboratory
October 22, 2024


UNIFI 1-MW Demo Objective

- There is a lack of standard testing protocols for grid-forming (GFM) inverters.
 - Develop standard testing protocols to understand the performance of GFM inverters.
- Explore the interoperability and functionalities of GFM inverters.
 - Test the key operation functions and modes of GFM inverters.
 - Use findings to drive GFM specifications.
- Provide findings and guidelines for industry and academia.
 - Utility: How to configure and control GFM inverters?
 - Vendor: What are the specs of GFM inverters?
 - Academia: What are the research gaps and key challenges?

Goal: Illustrate the interoperability guidelines at work with multiple vendors.



High-Level View of the Test Plan

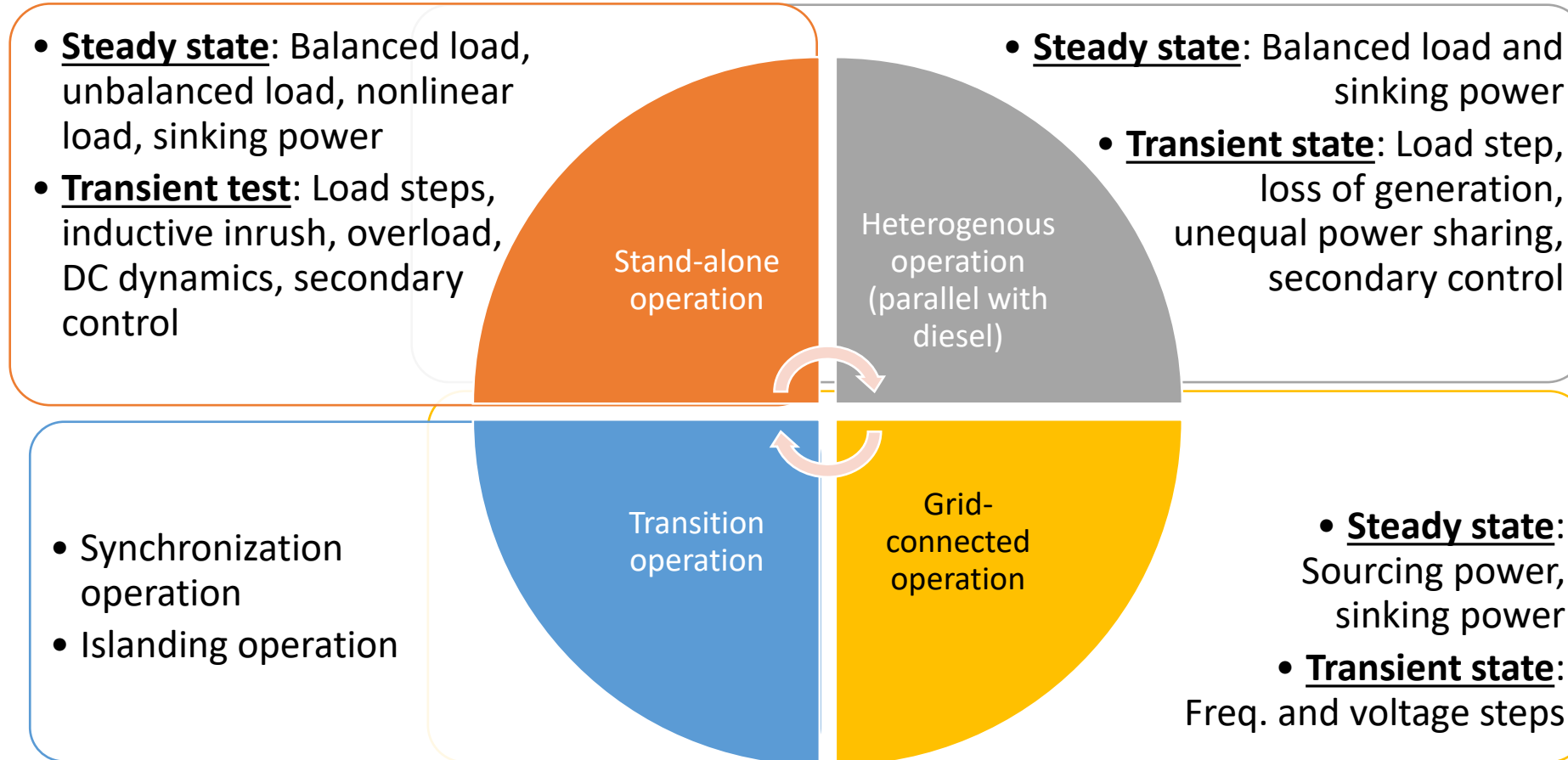


- **Steady state:** 5%, 10%, 25%, 50%, 75%, 100%, PF=1, 0.8 lagging and leading, pure inductive and capacitive loads
- **Transient state:** 25%, 50%, 75% and 100% PF=1, 0.8 lagging and leading
- **Transition operation:** 50% PF=1, 0.8 lagging and leading

Inverter Specifications

Specification	GFM#1	GFM#2	GFM#3	GFM#4	GFM#5
Frequency droop settings	0.25%	0.1 Hz gives 7.8 kW at 500	0.5 Hz	50, GFM droop W/P proportional Gain (Hz/W)	n/a (no droop, isochronous mode is configured and cannot change it)
Frequency droop	0.25%	0.67%	0.83%	0.83% (actually 0.35%)	
Voltage droop settings	5%	10 V gives 7.22 kVAR for 2160	24 V	2500, GFM droop V/Q proportional Gain (Vrms/Var)	
Voltage droop	5%	6.48%	5%	6.8%	
Synch check	Yes (GCB and MCB)	No	Yes (GCB)	Yes (GCB)	Yes (GCB)
Secondary control	Yes	Yes	Yes	Yes	No
Operation mode	GFM, GFL, and grid-supporting control	GFL and GFM control	GFL and GFM control	GFM, GFL, and grid-supporting control	Only GFM control
Communication protocol	Modbus TCP/IP			Modbus RS485	HTTP (REST command)

Testing Circuit

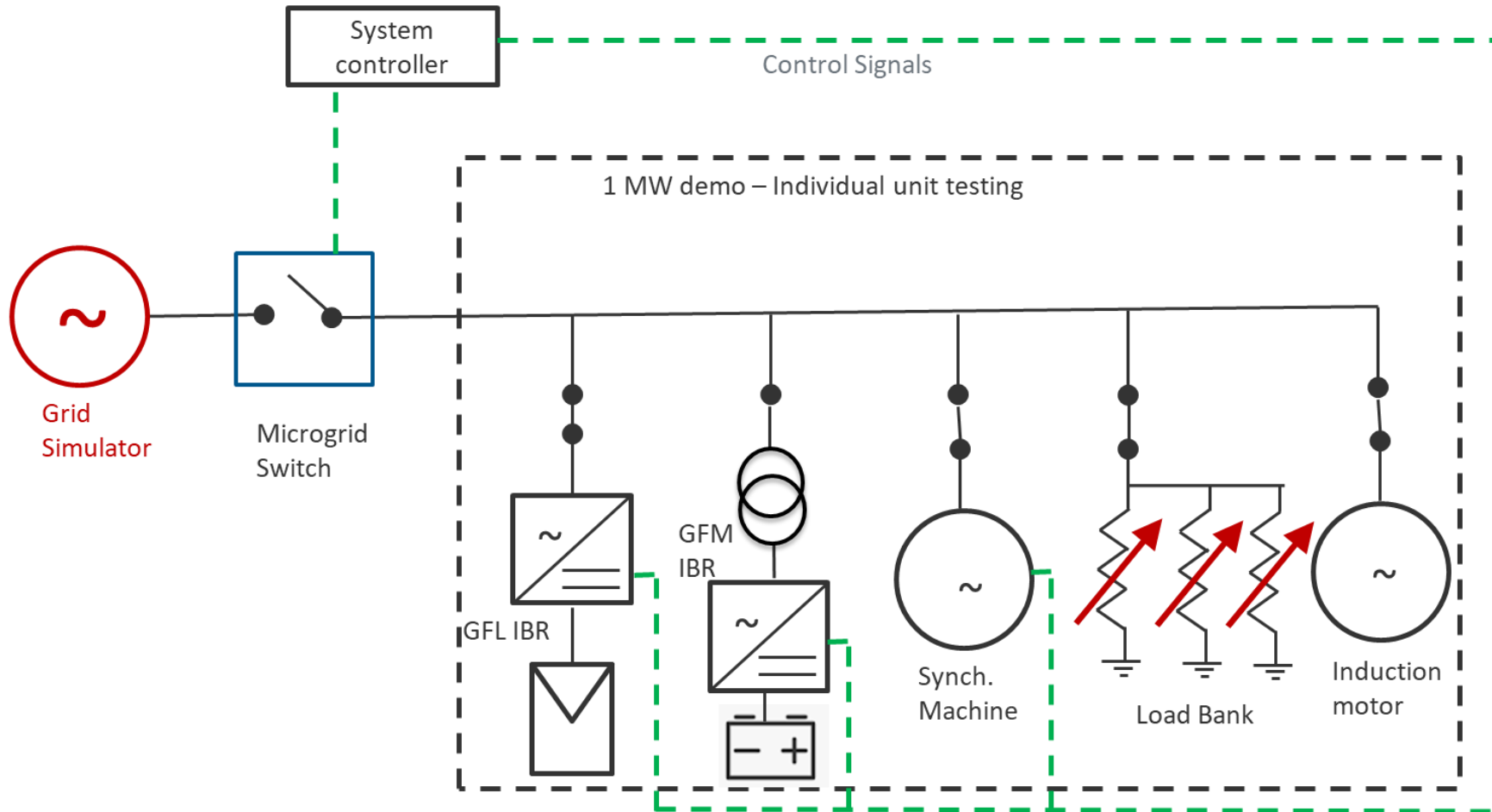

- The same testing circuit for easy configuration and testing
- The same testing protocol for fair comparison:
 - Power quality
 - Overloading capability
 - Transient stability.
- A system controller to dispatch all the elements


Characterization of Droop (f-p)

- Testing conditions

- PF1 load with 5%, 10%, 25%, 50%, 75%, and 100% loading of the capacity of the GFM inverter.
- Record the frequency and active power (p.u.).
- Plot the relationship between the active power (x-axis) and the frequency (y-axis)
- Characterize the relationship mathematically with a fitting function.

- Testing results

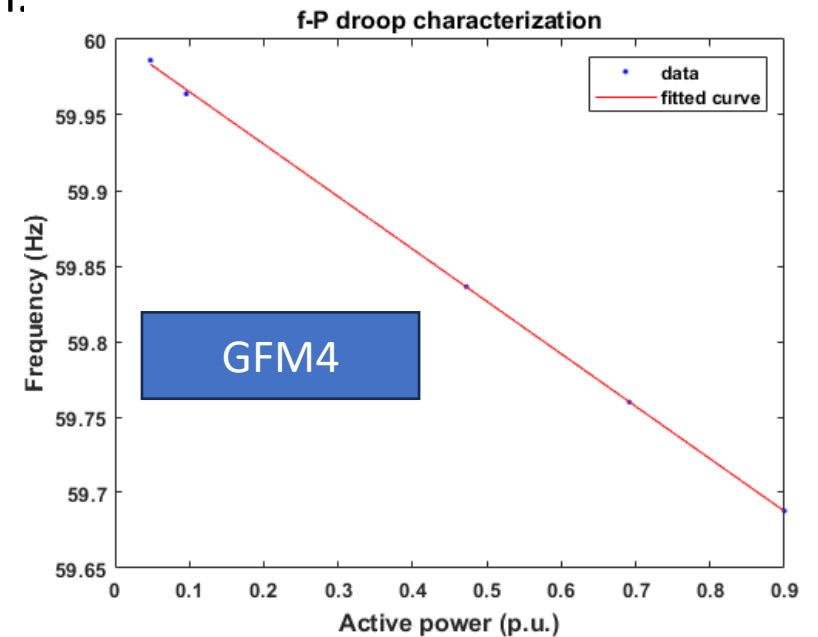- GFM inverters 1, 2, and 3 have the correct droop characterization as the setting value.
- GFM 4 has a misaligned droop characterization compared to the setting values.
 - The experimentally characterized droop is smaller than the setting value.
 - Find the linear relationship between the actual droop parameters and the default setting (**resolve the problem!**).




$$f^* = 60 - 0.2054 * P \left(m = \frac{0.2054}{60} = 0.35\% \right)$$


Default is 0.83%.

Characterization of Droop (v-q)


GFM 1 voltage droop characterization

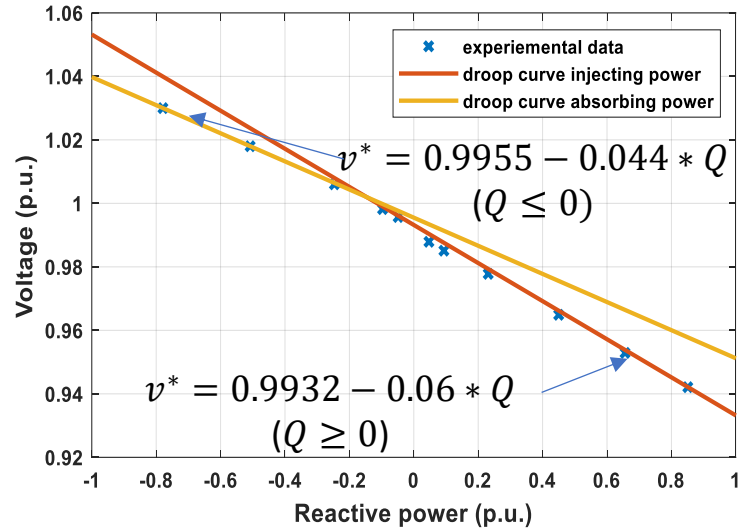


GFM 2 voltage droop characterization

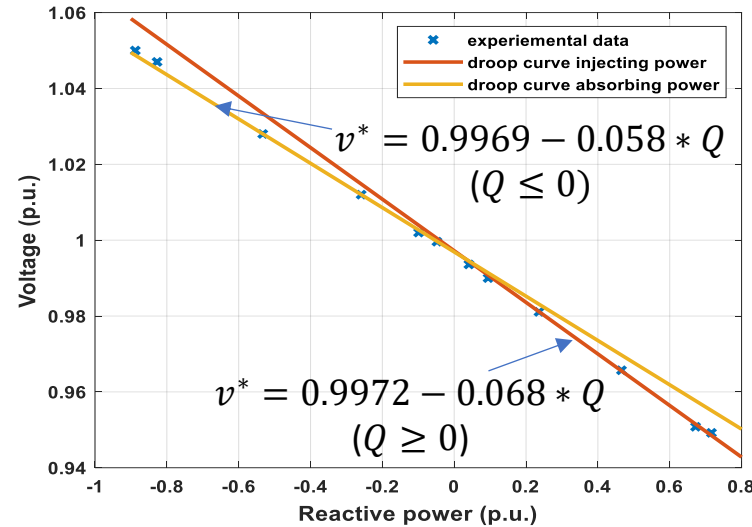

GFM 3 voltage droop characterization

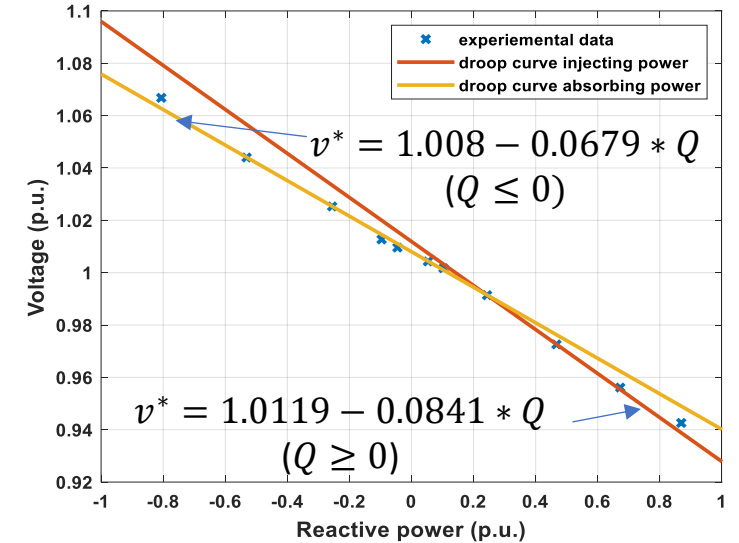

GFM 4 voltage droop characterization

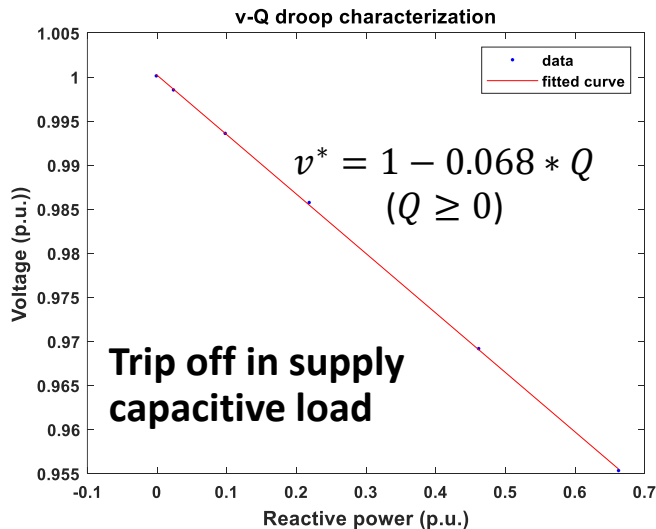

Learnings and findings:

- Not all GFM inverters have voltage droop coefficients that are the same as the defined value.
 - There are different droop characteristics in injecting and absorbing Q:
 - Injecting reactive power: The intercept is lower than “1” p.u., and the droop slope is higher than the defined value.
 - Absorbing reactive power: The intercept is lower than “1” p.u., and the droop slope is lower than the defined value.


Black Start

Inverter	Results description	Pass/fail
GFM#1	<ul style="list-style-type: none">The inverter dose not have a soft black start. The voltage has a peak of 1.4 p.u., and reach steady state after 0.15 secondsFor 50% and 100% load connection, the inverter reaches steady state within less than 2 cycles	Pass
GFM#2	<ul style="list-style-type: none">The inverter has a soft black start. The voltage reaches steady state after less than 0.1 secondsFor 50% and 100% load connection, the inverter reaches steady state within less than 2 cycles	Pass
GFM#3	<ul style="list-style-type: none">The inverter has a soft black start. The voltage reaches steady state after 4.88 secondsFor 50% and 100% load connection, the inverter reaches steady state within less than 2 cycles	Pass
GFM#4	<ul style="list-style-type: none">The inverter has a soft black start. The voltage reaches steady state after 0.1 secondsFor 50% and 100% load connection, the inverter reaches steady state within less than 2 cycles	Pass
GFM#5	<ul style="list-style-type: none">The inverter has a soft black start. The voltage reaches steady state after 0.1 secondsFor 50% and 100% load connection, the inverter reaches steady state within less than 2 cycles	Pass



Dispatching GFM Inverters

Grid-Connected Operation


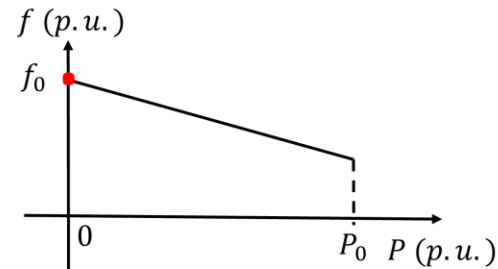
Scenario #1: both are 60 Hz, no power flow



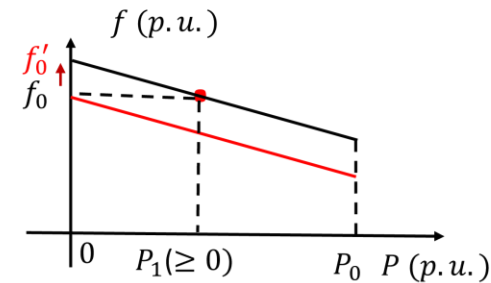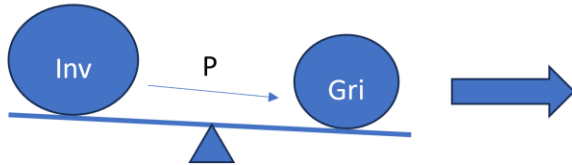Scenario #2: inverter shifts up the **frequency droop intercept**, active power flows from the inverter to the grid side.



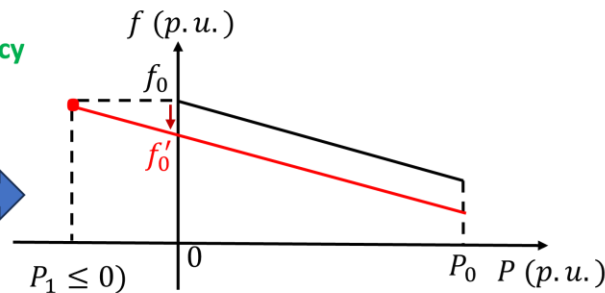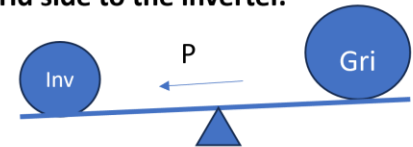
Scenario #3: inverter shifts down the **frequency droop intercept**, active power flows from the grid side to the inverter.



Inv: inverter; Gri: grid

$$f^* = 60 + \Delta f = 60 + m * P * 60$$

Islanded Operation

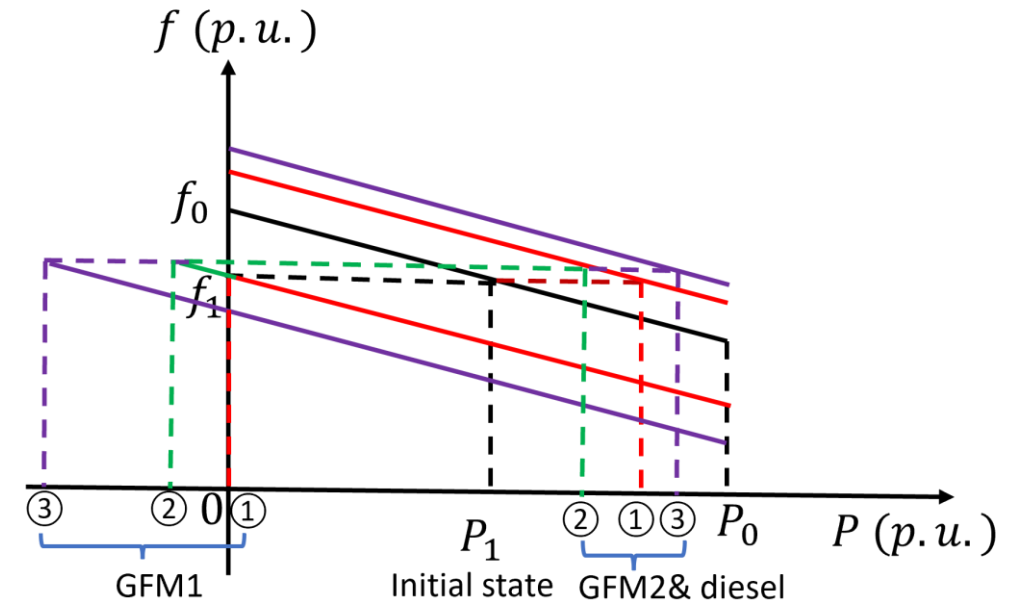

Start with equal power sharing:





- ① GFM 1 goes to zero power.
- ② Bring in grid-following (GFL).
- ③ Charge GFM 1.

$$\Delta f = (P_{new} - P_{old}) * m * 60$$

Dispatching GFM Inverters—Grid-Connected Mode

Testing conditions and procedures:

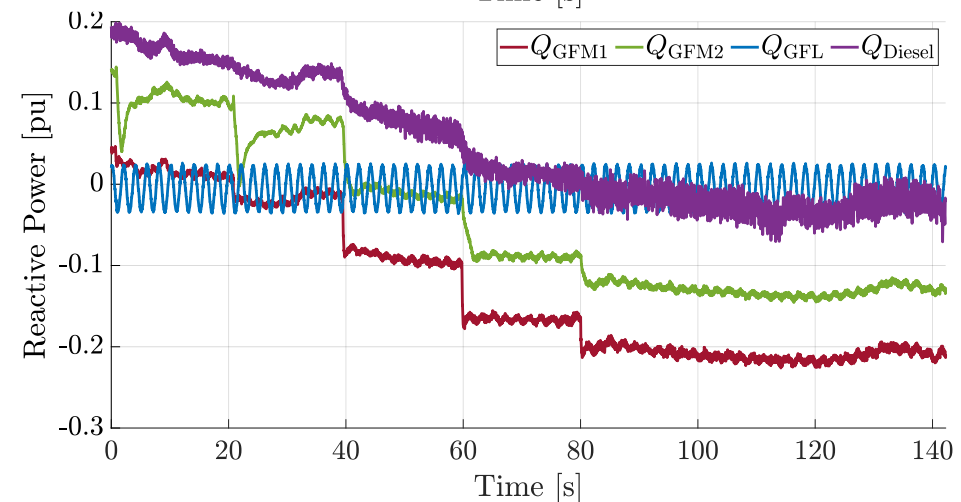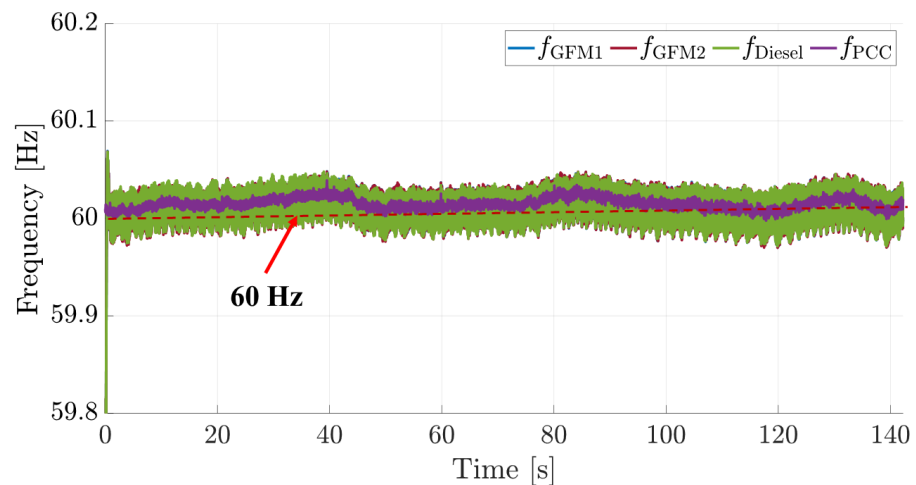
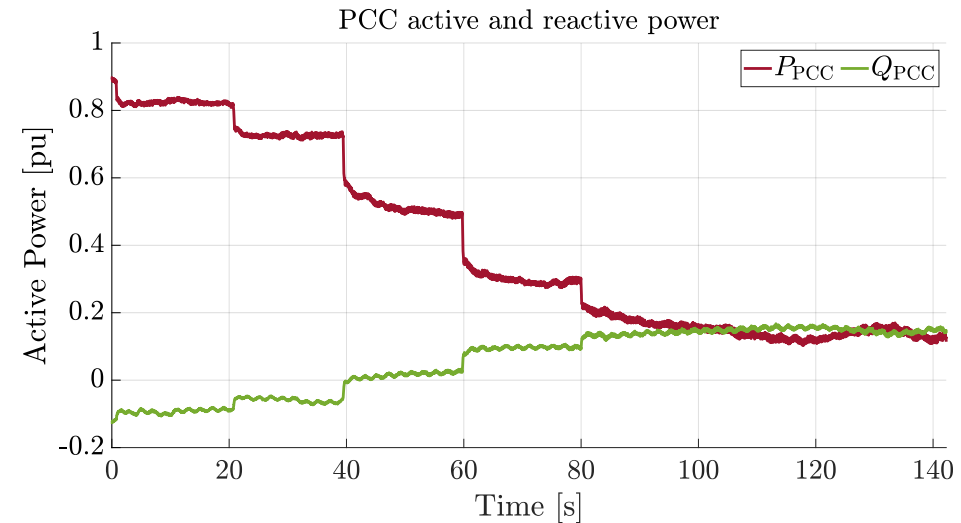
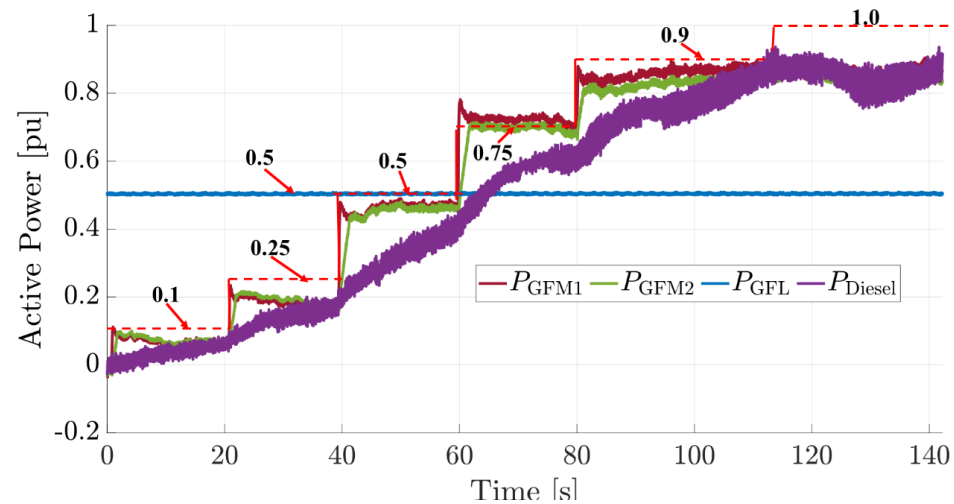
- The utility grid is used instead of the grid simulator, PF1 load and GFL with 50% dispatch.
- Dispatch each GFM source to the target power (5%, 10%, 25%, 50%, 75%, and 100%).









Dispatching GFM Inverters—Islanded Mode

Testing procedures:

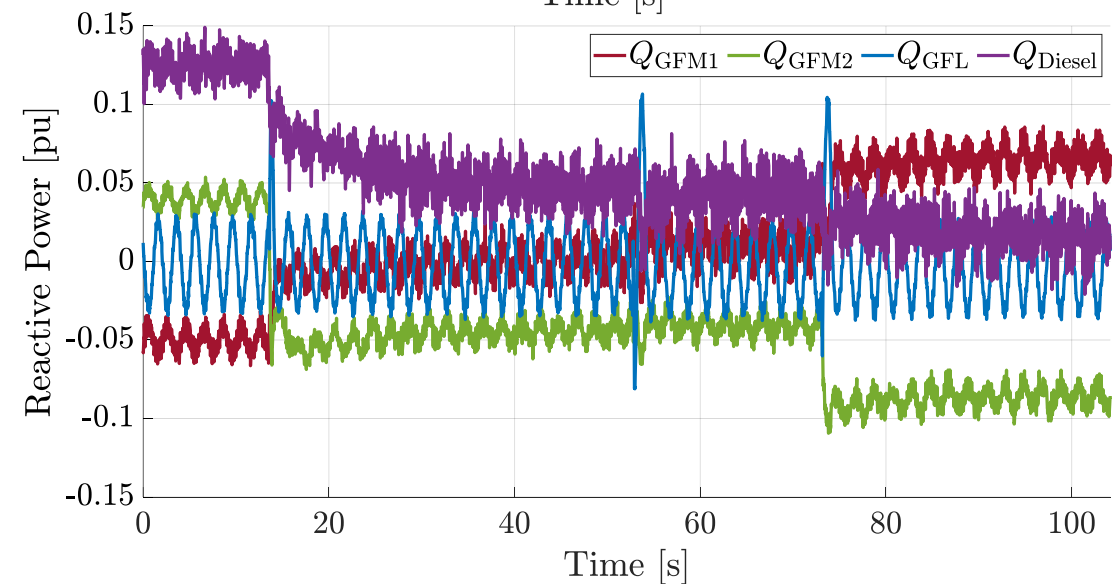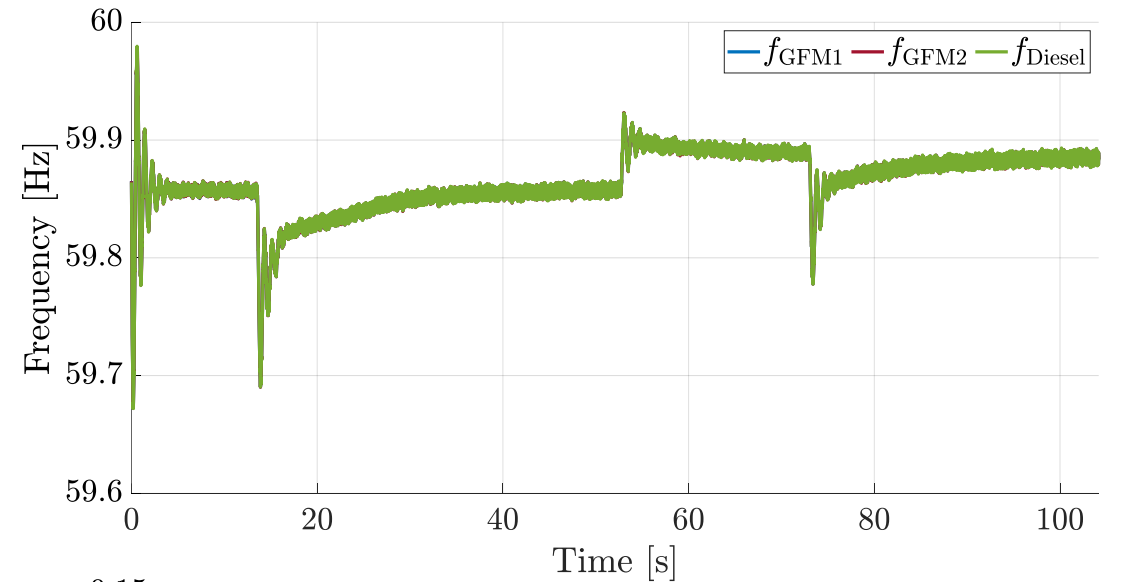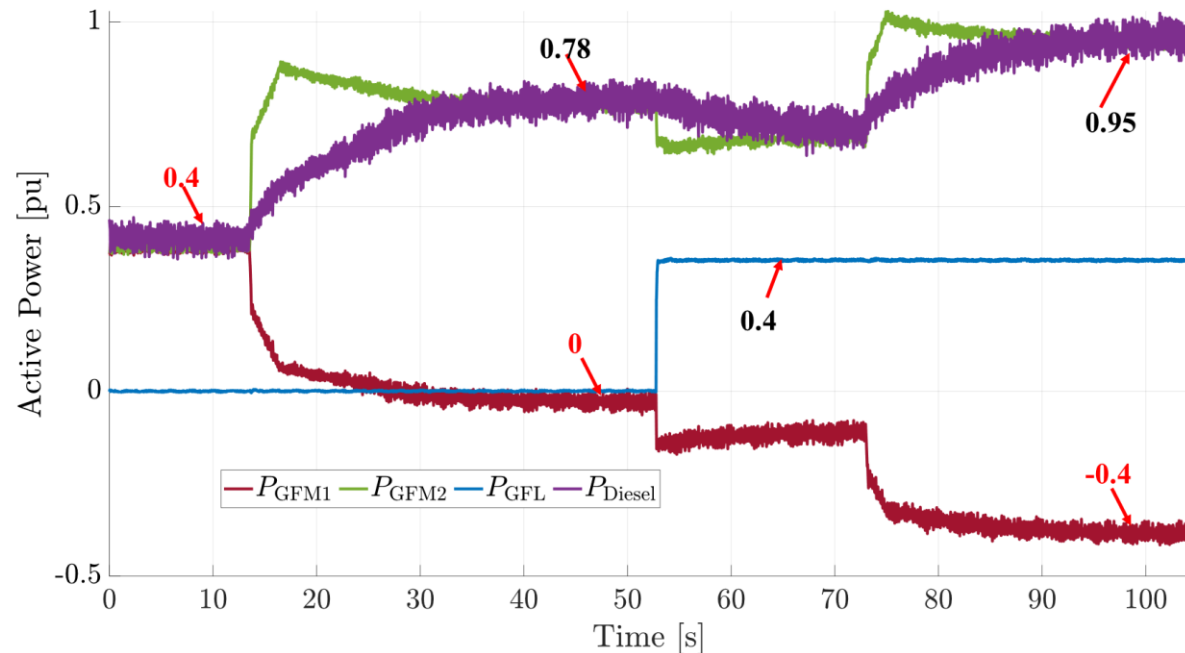- Objective: Start from equal power sharing to charge GFM 1 with 40% power.
- Strategy: ① Let the GFM output zero active power by dispatching GFM 2 and diesel; ② bring in GFL; ③ dispatch GFM 2 and diesel to let GFM 1 charge to 40% power.




Rate of Change of Frequency (ROCOF) Test

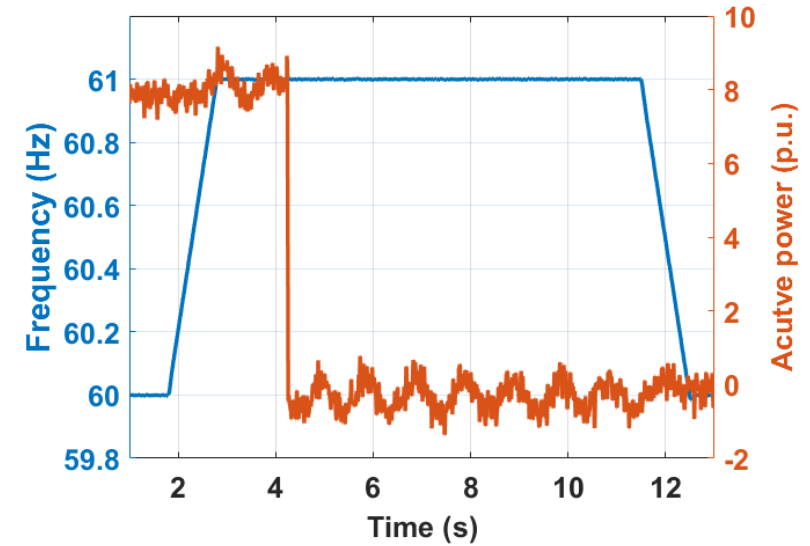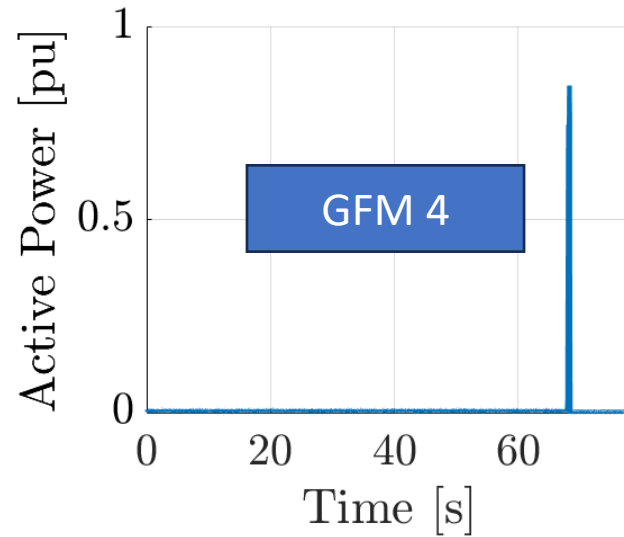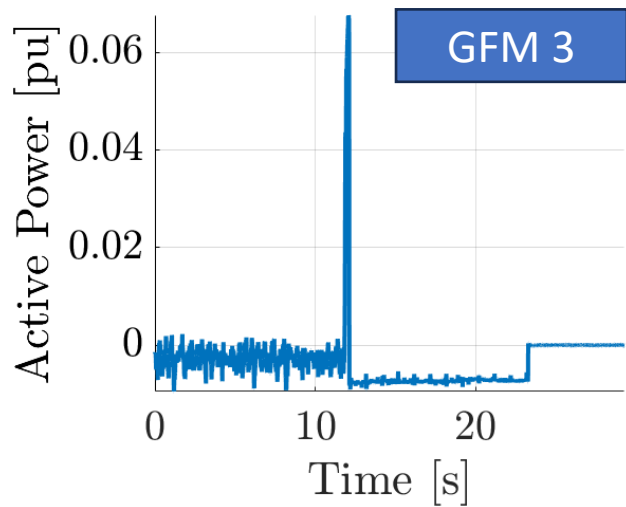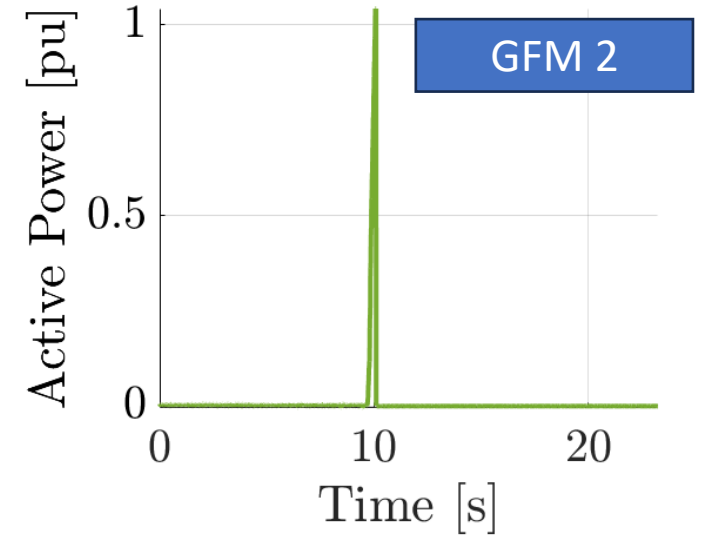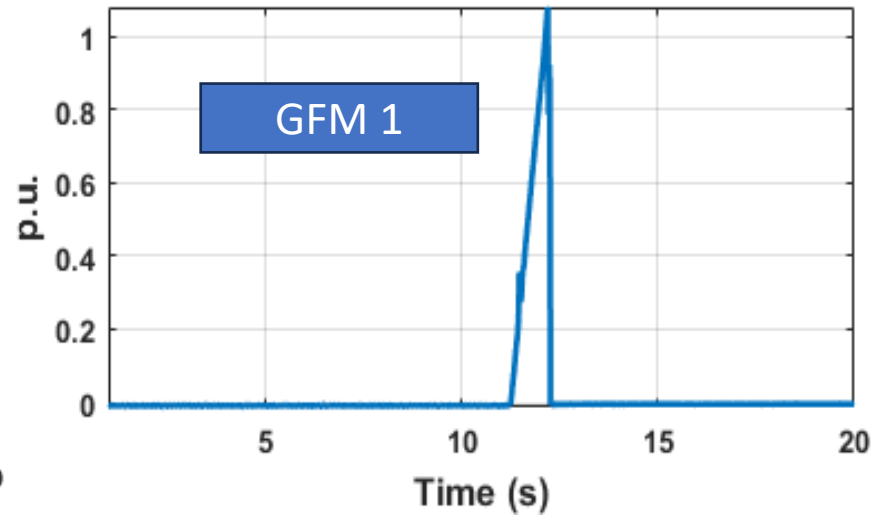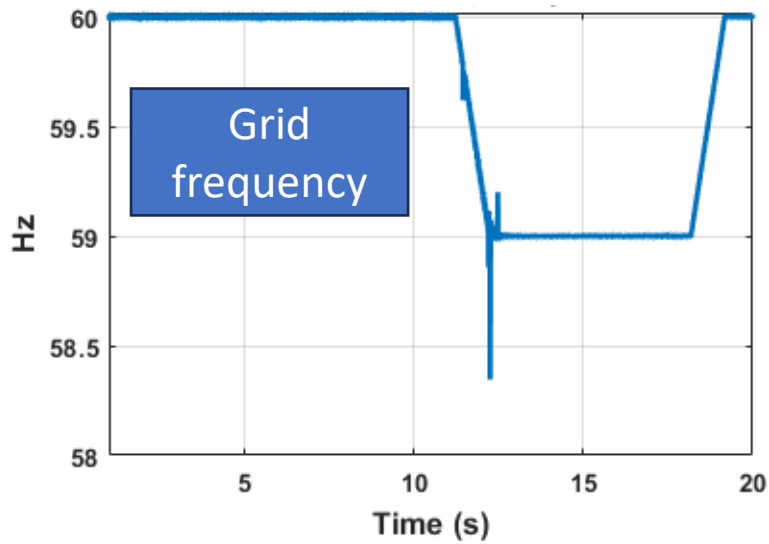


Troubleshooting for GFM 2


0.6% droop with 1.2-p.u. DC current

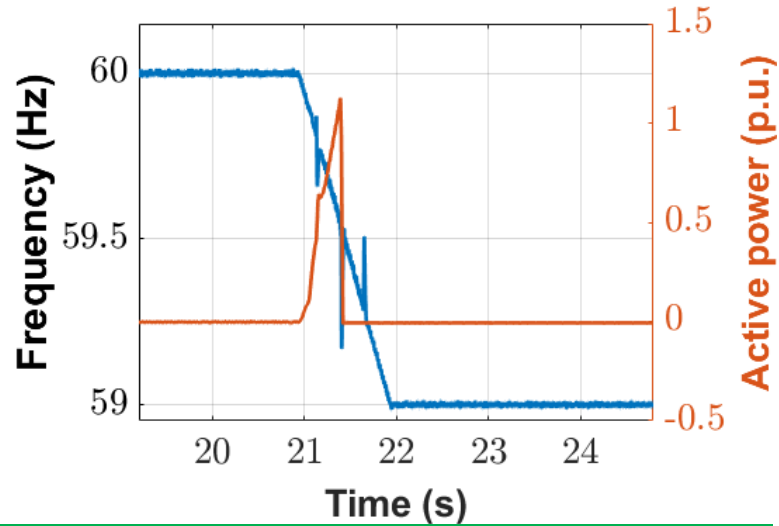


0.6% droop with 1.5-p.u. DC current

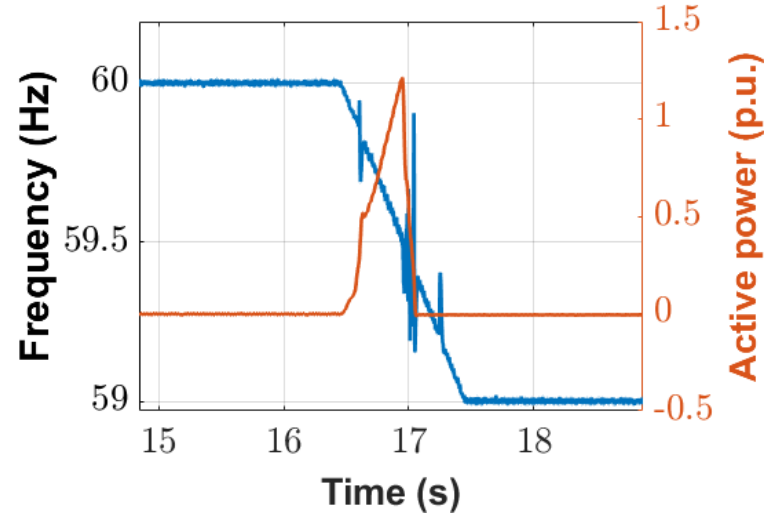

1.67% droop with 1.5-p.u. DC current

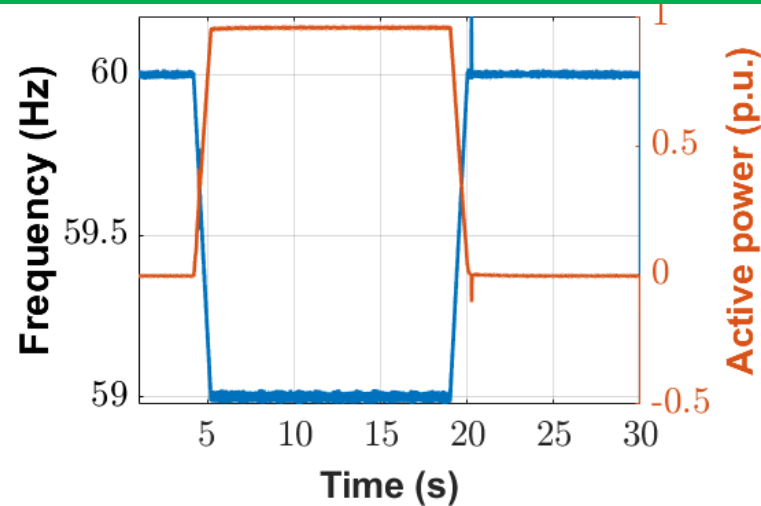

1.67% droop with 1.2-p.u. DC current

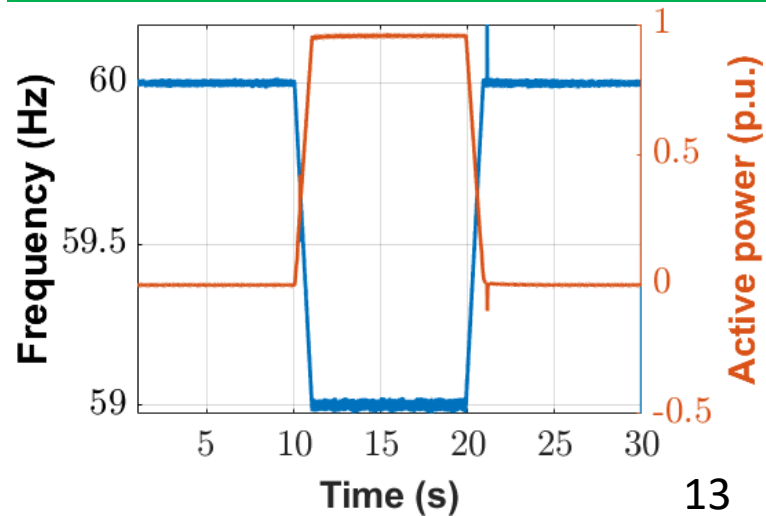


The DC side matters a lot! Cannot simply say that the inverter passed/failed the ROCOF test. The DC side capacity is important!

$$H = \frac{\Delta P \cdot f_0}{2S_{rating} \cdot 1 \text{ Hz/s}}$$

$$H = 0.475 \text{ kW s/kWVA}$$


Secondary Control—Frequency

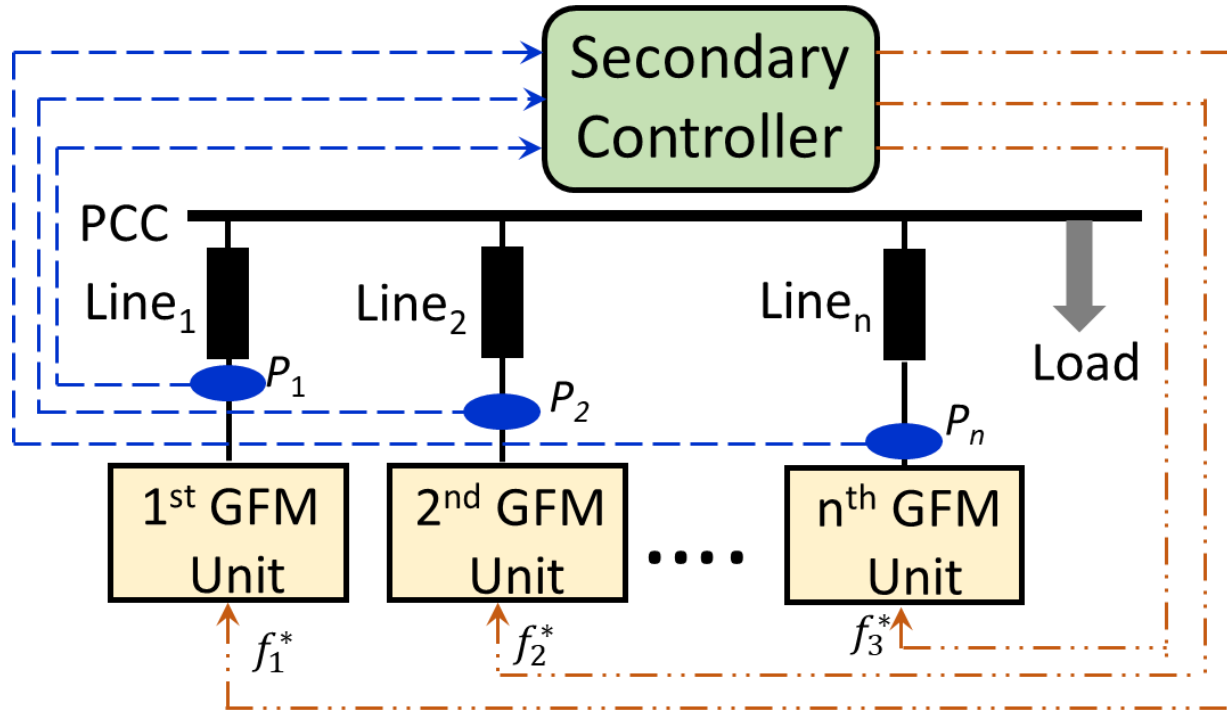



$$f_1^* = f_2^* = f_3^* = 60 + m * P * 60 \quad (m \text{ is the droop percentage})$$

Testing results:

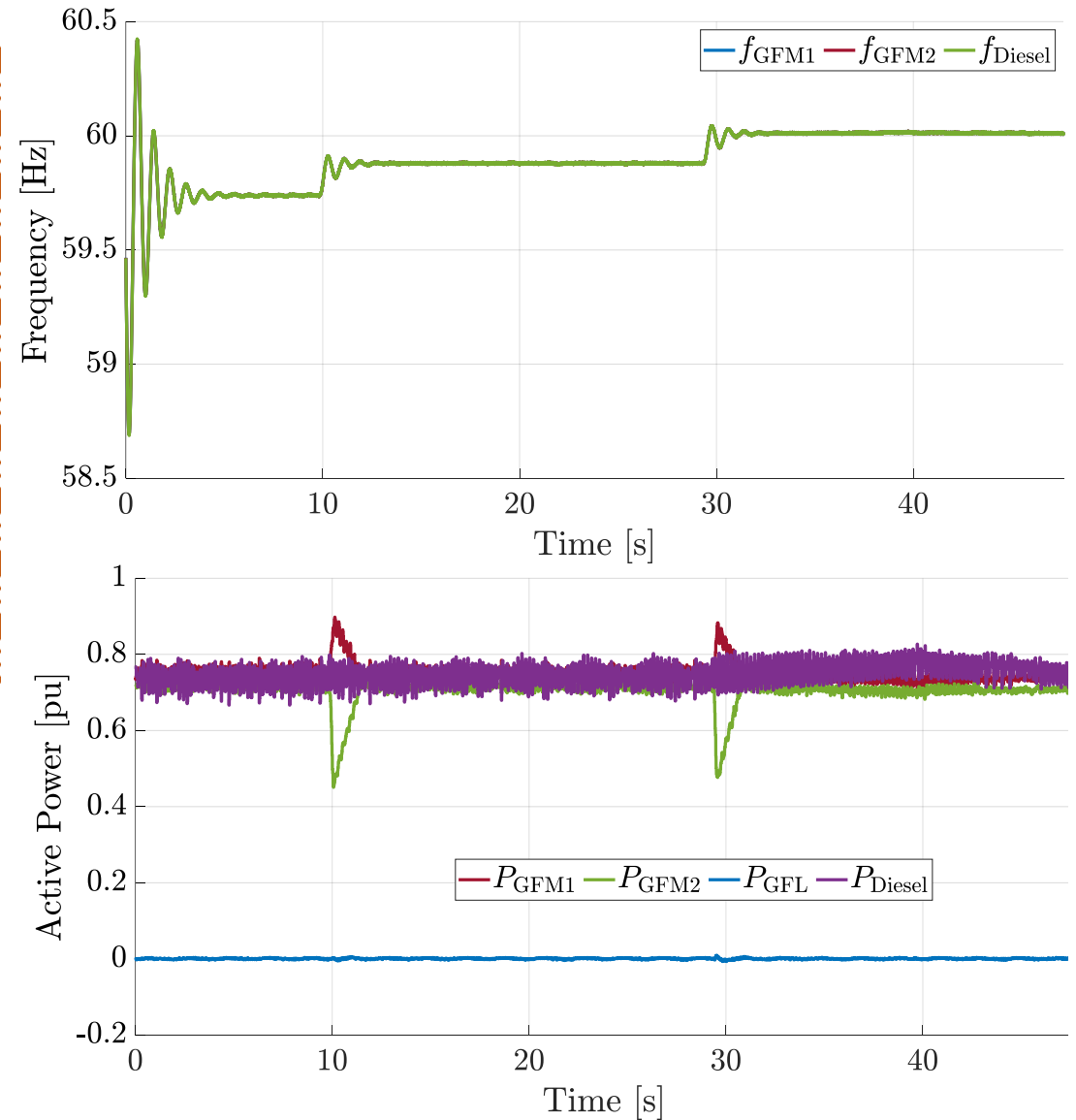- The frequency is regulated to the nominal values.
- No competing effect and all regulate into the nominal frequency.





Secondary Control—Voltage

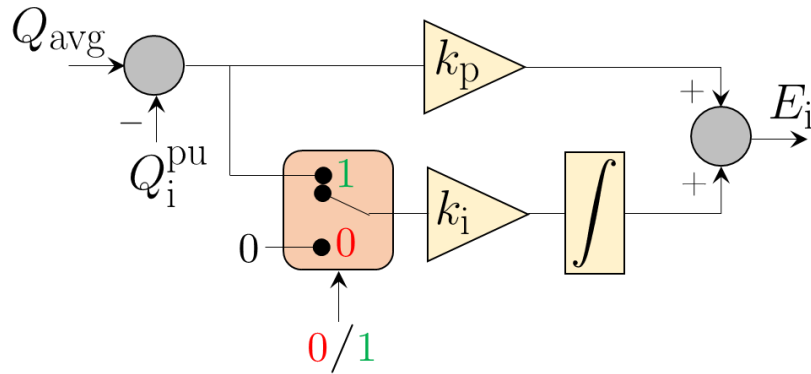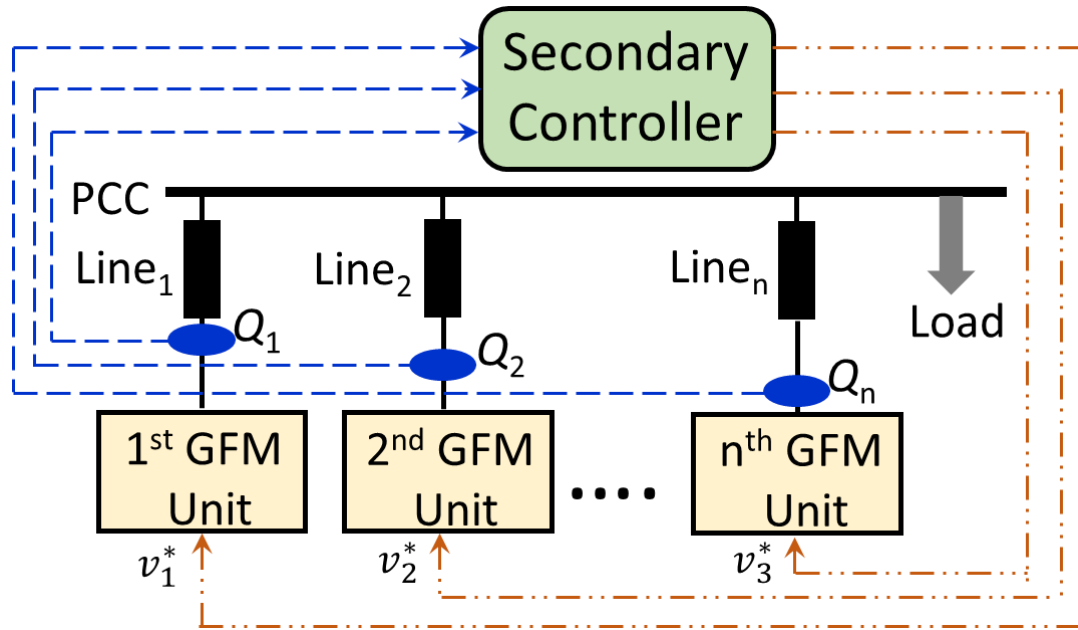

$$v_i^* = v^* - n * Q + E_i$$
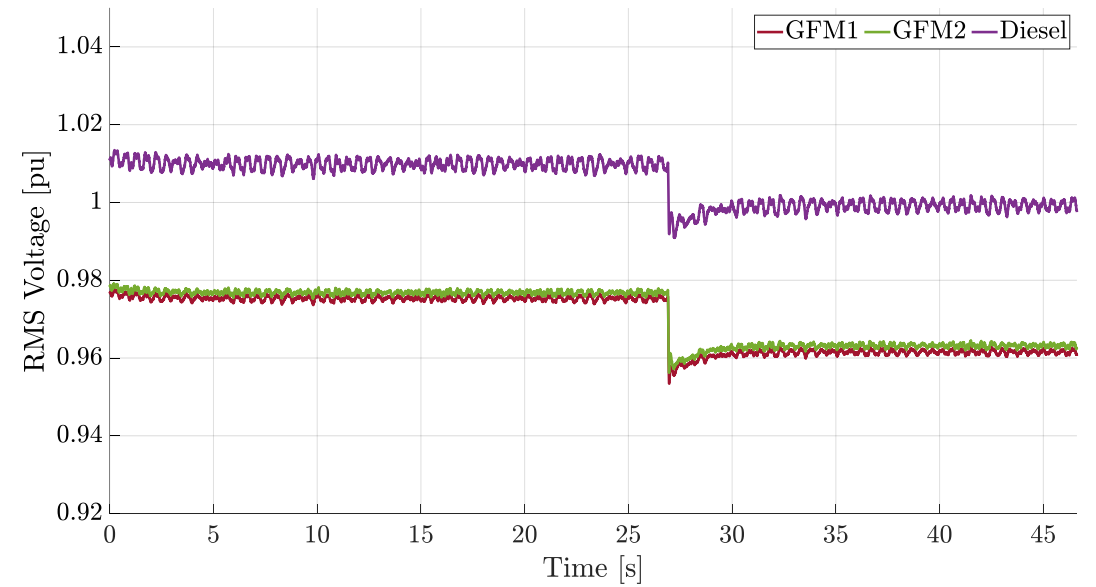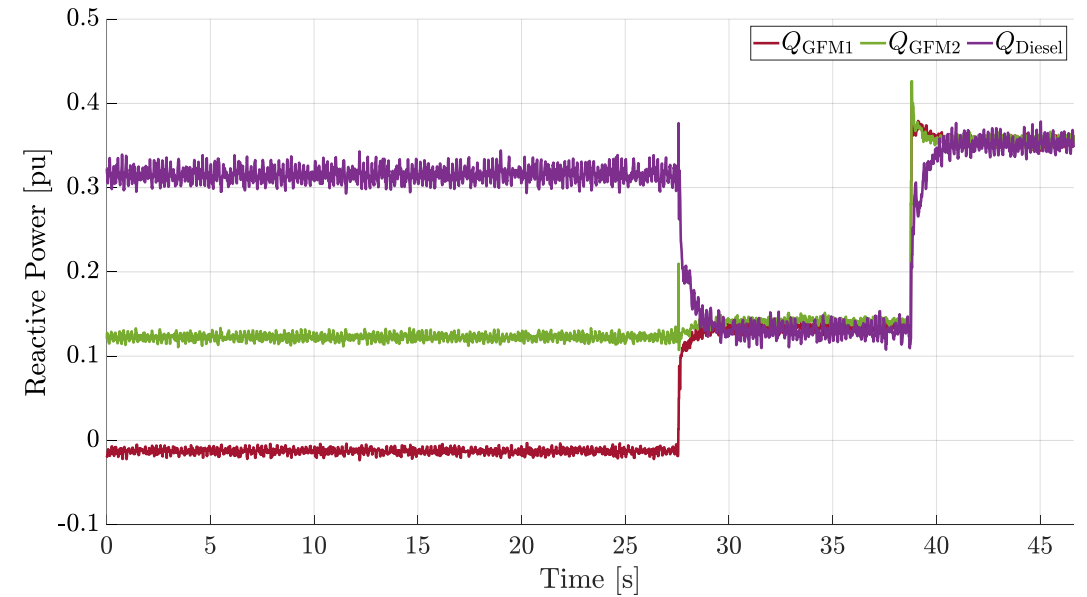
$$Q_{avg} = \frac{1}{n} \left(\frac{Q_1}{S_1} + \frac{Q_2}{S_2} + \dots + \frac{Q_n}{S_n} \right)$$



Overview of ESIF Lab



Grid simulator



PCC switch



Section 2



Section 4



Diesel



Section 1



Load bank




Section 3

Photos by NREL

Key Learnings and Findings

- Frequency and voltage droop need to be characterized.
 - There are different droop languages that should be unified.
- Tuning the droop slope can easily cause (or prevent) stability issues.
- Through adjusting the inverter droop intercept, we can:
 - Perform secondary control.
 - Dispatch the GFM inverter to output the desired power.
 - **Dispatch GFM inverters like we dispatch GFL inverters** (in parallel with diesel and grid-connected operation).
- Reactive power sharing can be a problem—without proper control, the use of reactive power can unexpectedly de-rate the inverter output.
- GFM inverters have similar output impedance.

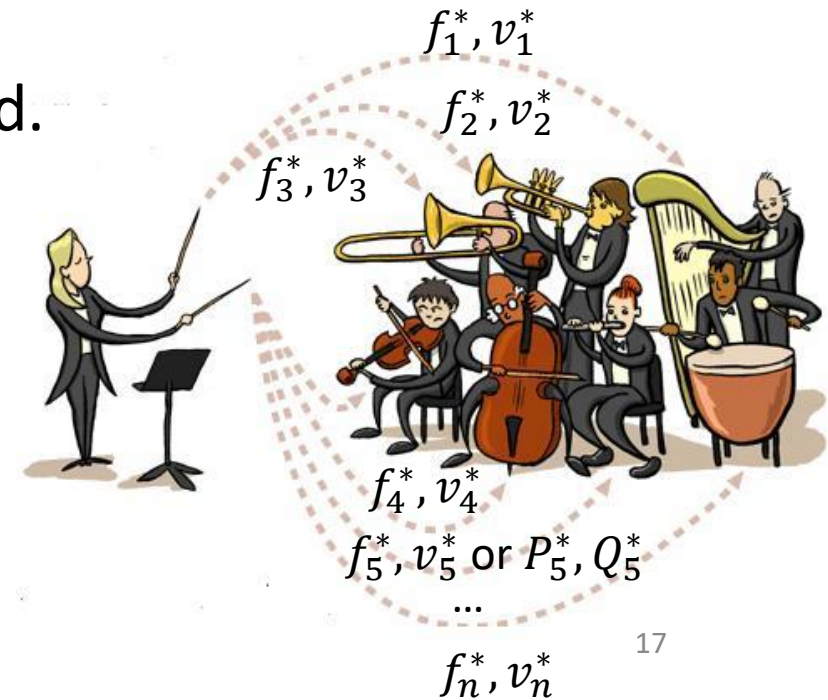

KEY FINDING:
Interoperability and
dispatch of GFM
inverters is all about
droop!

Thank you!



Photos by NREL

Acknowledgment: This material is based upon work supported by the U.S. Department of Energy’s Office of Energy Efficiency and Renewable Energy (EERE) under the Solar Energy Technologies Office Award Number 38637.

Disclaimer: This report was prepared as an account of work sponsored by an agency of the United States Government. Neither the United States Government nor any agency thereof, nor any of their employees, makes any warranty, express or implied, or assumes any legal liability or responsibility for the accuracy, completeness, or usefulness of any information, apparatus, product, or process disclosed, or represents that its use would not infringe privately owned rights. Reference herein to any specific commercial product, process, or service by trade name, trademark, manufacturer, or otherwise does not necessarily constitute or imply its endorsement, recommendation, or favoring by the United States Government or any agency thereof. The views and opinions of authors expressed herein do not necessarily state or reflect those of the United States Government or any agency thereof.